
Fall 2017 - Friday 13 (Spooky!)
 
### **Objectives**

The purpose of this lab is to design, synthesize, simulate and test a 32-bit ALU which handles addition, substraction, logic operations, load upper immediate, set less than, zero and overflow for on signed integers. The ALU will be built upon and used as part of a more complex CPU design in future labs.



## **Procedure**

This lab follows the procedure outlined in Parts I, II, III, and IV of the tutorial "Digital Logic Simulation and Synthesis Using Modelsim, Precision RTL, and Xilinx ISE". The end-goal is to simulate, synthesize and download to the Xilinx FPGA board the 32-bit ALU described below in the LAB 1 manual.


### Requirements

- 1) Implement the ALU using any style of VHDL
- 2) Support signed integer overflow and arithmetic
- 3) Single-cycle implementation
- 4) Satisfy the following "truth" table

func	output	Comments
00	у	used to implement the lui instruction
01	"000MSB" of adder_subttract	used for the slt (set less than zero) instruction
10	output of adder_subtract	x+y if add_sub = '0' x-y if add_sub = '1'
11	output of logic unit	x AND y if logic_func = "00 x OR y if logic_func = "01" x XOR y if logic_func = "10" x NOR y if logic_func = "11"

#### Results

My design:

 

I followed the **structural approach** (with port maps) to build my ALU for the following reasons:

**Testing->** It is easier to verify correctness of a 1 bit ALU which makes debugging easier if the design is broken into components (isolates errors between 1bit ALU logic, MSB ALU logic, connections)

**Reusability**-> 1 bit ALUs can be used to build N bit ALU by just combining in multiples, the 1bit ALU can also be used easily as part of another system

**Customization**-> Bit-level functionality can be made custom for certain bits by just using a different architecture for certain bits

**Optimization**-> it is easier to optimize 1 small component than to try to optimize the whole thing at the same time

**Synthesizer "decoupling"**-> The design is closer to "reality" which makes the final implementation less dependent on the synthesizer used

**Adaptability**-> The 1 bit ALU can later be modified to implement its function in a different way but overall the same behavior will be seen at the 32bit level

Furthermore, since I was not creating anything new I found this approach more intuitive as it implements a well-established design we learned in class. Certainly there are arguments in favor of different approaches as well.

#### alu4 Entity for alu1bit: add sub library IEEE; use IEEE.std logic 1164.all; carry\_in func(1:0) entity alu1bit is less logic\_func(1:0) -- input of 1bit alu a, b, less, carry\_in : in std\_logic; add\_sub : in std\_logic ; -- 0 = add , 1 = sub logic\_func : in std\_logic\_vector(1 downto 0 ) ; -- 00 = AND, 01 = OR , 10 = XOR , 11 = NOR func : in std\_logic\_vector(1 downto 0 ) ; -- 00 = lui, 01 = setless , 10 = arith , 11 = logic -- output of 1bit alu result : out std logic; carry out : out std logic end alu1bit ; alu31 **Entity for alu1bitmostsignificant:** add sub overflow library IEEE; use IEEE.std\_logic\_1164.all; camy in result. func(1:0) set entity alu1bitmostsignificant is ess logic\_func(1:0) -- input of 1bit alu most significant alu1 bitmostsignificant a, b, less, carry\_in : in std\_logic; add\_sub : in std\_logic ; -- 0 = add , 1 = sub logic\_func : in std\_logic\_vector(1 downto 0 ) ; -- 00 = AND, 01 = OR , 10 = XOR , 11 = NOR func : in std\_logic\_vector(1 downto 0 ); -- 00 = lui, 01 = setless , 10 = arith , 11 = logic --output of 1bit alu most significant result : out std\_logic; set : out std\_logic; overflow: out std\_logic end alu1bitmostsignificant ;

## Entity for alu32bit:

(forgot to take blackbox picture)

```
library IEEE;
use IEEE.std_logic_1164.all;
entity alu32bit is
    -- input of 32bit alu
    a, b : in std_logic_vector(31 downto 0);
                                               -- assuming SIGNED overflow logic, note:
                                               --possible to get overflow even if you don't have output carry bit
                                               -- (so overflow logic should be done here or in MSB? by checking signs
    --a is x, b is y
    add_sub : in std_logic ; -- 0 = add , 1 = sub
    logic func : in std logic vector(1 downto 0 ); -- 00 = AND, 01 = OR , 10 = XOR , 11 = NOR
    func : in std_logic_vector(1 downto 0 ) ; -- 00 = lui, 01 = setless , 10 = arith , 11 = logic
    -- output of 32bit alu
    result : out std_logic_vector(31 downto 0) ;
   overflow : out std_logic ;
    zero : out std_logic
);
end alu32bit ;
```

# Architecture of alu1bit:

```
architecture lab1 of alu1bit is
begin
    main: process (a, b, less, carry_in, add_sub, logic_func, func)
        -- switch based on func
        case func is
            when "00" => --lui
               result <= b;
                carry_out <= '0'; --no carry
            when "01" => --setless
                result <= less;
                carry_out <= (a AND (NOT b)) OR (a AND carry_in) OR ((NOT b) AND carry_in);</pre>
                --because we're doing substraction during setless,
                -- the carry in will be '1' for the LSB (see carry in hack)
            when "10" => --arith (1-bit, 2's complement based)
                         -- (add_sub decides if we invert b,
                         --carry_in will be 0 for the LSB for addition and 1 during substraction)
                result <= a XOR (b XOR add_sub) XOR carry_in;
                carry_out <= (a AND (b XOR add_sub)) OR (a AND carry_in) OR ((b XOR add_sub) AND carry_in);
                -- (b XOR add_sub) means invert b if add_sub is 1 (i.e. doing sub);
            when "11" => --logic (bit-wise, carries don't exist)
                case logic func is
                    when "00" => --and
                        result <= a AND b;
                        carry_out <= '0';
                    when "01" => --or
                       result <= a OR b;
                       carry_out <= '0';
                    when "10" => --xor
                        result <= a XOR b;
                        carry out <= '0';
                    when "11" => --nor
                        result <= a NOR b;
                        carry_out <= '0';
                    when others =>
                       result <= '0';
                       carry_out <= '0';
                end case;
            when others =>
                result <= '0';
                carry out <= '0';
        end case;
    end process;
end lab1;
```

## Architecture of alu1bitmostsignificant:

The MSB is simply a alu1bit with added set and overflow logic:

```
architecture lab1 of alu1bitmostsignificant is
-- reuse alu1bit implementation
component alu1bit
    port(
       a, b, less, carry_in, add_sub: in std_logic;
       logic_func : in std_logic_vector(1 downto 0 ) ;
       func : in std logic vector(1 downto 0 ) ;
       result, carry out : out std logic
    );
    end component;
    --extending functionality of alu1bit
    signal last_carry: std_logic;
    signal temp_result: std_logic;
begin
    --MSB alu works like alu1bit... but has extra features
    MSB: alu1bit
    port map (a => a, b => b, less => less, carry_in => carry_in,
              add_sub => add_sub, logic_func => logic_func, func => func,
             result => temp result, carry out => last carry);
    result <= temp_result;
    -- setlessthan bit logic
    set <= a XOR (NOT b) XOR carry_in; --the MSB from substraction result is "set" to "less" at the LSB
    msb_extra: process (carry_in, last_carry, func) --, a, b, add_sub, temp_result)
    begin
        -- overflow logic
       if (func = "10") then -- arith
           overflow <= carry_in XOR last_carry;</pre>
        else
           overflow <= '0';
        end if;
    end process;
end lab1;
```

### Architecture of alu32bit:


### As you may imagine, a lot of port maps are incoming

```
architecture lab1 of alu32bit is
    constant logic 0: std logic:= '0';
    signal carries: std_logic_vector(30 downto 0); --vector holding carries of addition/substraction
    --taken from MSB and fed into LSB, if func is '01' (setless), it will be selected to signal temp_result: std_logic_vector(31 downto 0); --holds results of all 1bit ALUs, used to compute Zero and LUI result masking signal carry_in_hack: std_logic := '0'; -- carry_in needs to be 1 for subs and for setless /01'
                                                              --taken from MSB and fed into LSB, if func is '01' (setless), it will be selected into result(0)
    component alu1bit
         a, b, less, carry_in, add_sub: in std_logic;
         logic_func : in std_logic_vector(1 downto 0 ) ;
func : in std_logic_vector(1 downto 0 ) ;
         result, carry_out : out std_logic
    end component;
    component alu1bitmostsignificant
        a, b, less, carry_in, add_sub: in std_logic;
         logic_func : in std_logic_vector(1 downto 0 ) ;
func : in std_logic_vector(1 downto 0 ) ;
         result, set, overflow : out std logic
     end component;
    begin
         -- hacky, but carry_in needs to be 1 for subs and for setless (01)
         carry_in_hack <= add_sub OR func(0);</pre>
         -- if result is 000...000, zero is 1 else 0
         zero <= NOT( temp_result(0) OR temp_result(1) OR temp_result(2) OR temp_result(3)</pre>
                      OR temp_result(4) OR temp_result(5) OR temp_result(6) OR temp_result(7) OR temp_result(8) OR temp_result(10) OR temp_result(11) OR temp_result(11)
                      OR temp_result(12) OR temp_result(13) OR temp_result(14) OR temp_result(15) OR temp_result(16) OR temp_result(17) OR temp_result(18) OR temp_result(19) OR temp_result(20) OR temp_result(21) OR temp_result(22) OR temp_result(23)
                      OR temp_result(24) OR temp_result(25) OR temp_result(26) OR temp_result(28) OR temp_result(29) OR temp_result(30) OR temp_result(31));
         -- nortman each 1hit together to form 32hit alu
         alu0: alu1bit --less is connected to the set_bit coming from MSB --carry_in '1' when doing sub or slt
         alu1: alu1bit --less is '0' always except LSB
                            -carry_in of following 1bitALU is carry_out of previous one
         port map (a => a(1), b => b(1), less => logic_0, carry_in => carries(0),
                  add_sub => add_sub, logic_func => logic_func, func => func, result => temp_result(1), carry_out => carries(1));
             .....port maps of bits 2 to 29......
         alu30: alu1bit
         port map (a => a(30), b => b(30), less => logic_0, carry_in => carries(29),
                    add_sub => add_sub, logic_func => logic_func, func => func, result => temp_result(30), carry_out => carries(30));
          -overflow is decided at the MSB, the set bit is routed to the LSB alu and used during the setless than func-
         alu31: alu1bitmostsignificant
         port map (a => a(31), b => b(31), less => logic_0, carry_in => carries(30),
                   add_sub => add_sub, logic_func => logic_func, func => func, result => temp_result(31), overflow => overflow, set => set_bit);
          --special case
         alu32bitproc : process(func, temp result)
              if (func = "00") then --lui
                   result <= temp_result AND "11111111111111111110000000000000"; --mask lowest 16bits during LUI
                 result <= temp_result;
```


end lab1;

end if;


# Synthesized circuit:

 

# Another view of synthesized circuit:

 


# Technology mapped circuit:

 

# **Simulation Results**


## <u>ADD</u>
 
#arith #arith ADD force add_sub 0 force func 10 force a 00000000000000000000000000000000000
#arith #arith ADD force add_sub 0 force func 10 force a 00000000000000000000000000000000000
#arith #arith ADD with overflow force add_sub 0 force func 10 force a 010000000000000000000000000000000000
#arith #arith ADD force add_sub 0 force func 10 force a 11111111111111111111111111111111111
#arith #arith ADD with overflow force add_sub 0 force func 10 force a 011111111111111111111111111111 force b 00000000000000000000000000000000000



 
### **LOGIC**


```
#logic
#logic AND
force func 11
force logic func 00
force a 00000000000000000000000000001111
run 2
#logic
#logic OR
force func 11
force logic func 01
force b 0000000000000000000000000001111
run 2
#logic
#logic XOR
force func 11
force logic func 10
force a 00000000000000000000000000001111
force b 00000000000000000000000000001011
run 2
#logic
#logic NOR
force func 11
force logic func 11
run 2
```



### <u>LUI</u>

 

 
#setless true force func 01 force a 110000000000000000000000000000011 #setless true force func 01 force b 01000000000000000000000000000011 run 2 #setless false force func 01 force b 0000000000000000011111111111111 run 2 #setless false force func 01 run 2 force func 01 run 2



#### **SUB**
 
#arith #arith SUB force add sub 1 force func 10 run 2 #arith #arith SUB with overflow force add sub 1 force func 10 run 2 #arith #arith SUB force add sub 1 force func 10 run 2 #arith #arith SUB with overflow force add\_sub 1 force func 10 run 2



# Configuration file (I/O mapping):

```
NET a(2) LOC = N5;
NET a(1) LOC = L4;
NET a(0) LOC = N2;
NET b(2) LOC = R9;
NET b(1) LOC = M3;
NET b(0) LOC = P1;
NET add sub LOC = N3;
NET func(1) LOC = AF9;
NET func(0) LOC = AF8;
NET logic_func(1) LOC = AD11;
NET logic func(0) LOC = AC11;
NET zero LOC = AC4;
NET overflow LOC = AA5;
NET result(7) LOC = P2;
NET result(6) LOC = R7;
NET result(5) LOC = P4;
NET result(4) LOC = T2;
NET result(3) LOC = R5;
NET result(2) LOC = R3;
NET result(1) LOC = V1;
NET result(0) LOC = T6;
```

### Human explanation of mapping:

```
a(31,30,29):
               red switch(dip) 1,2,3
b(31,30,29):
               red switch(dip) 4,5,6
add_sub:
               red_switch 8
func(1,0):
               blue_switch 3,2
logic_func(1,0): blue_switch 1,0
zero:
               small led 0
overflow:
               small_led 3
output(31,30,29,28): red_led(left to right)
                       green_led(left to right)
output(3,2,1,0):
```

### **NOTES:**

```
switch up = logic 0
switch down = logic 1
LEDs are active LOW (logic 0 = ON)
```

### Precision.log file:

```
# Info: [9566]: Logging session transcript to file /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/precision.log
// Precision RTL Synthesis 64-bit 2016.1.0.15 (Production Release) Wed Jun 8 09:35:56 PDT 2016
// Copyright (c) Mentor Graphics Corporation, 1996-2016, All Rights Reserved.
                Portions copyright 1991-2008 Compuware Corporation UNPUBLISHED, LICENSED SOFTWARE.
11
                CONFIDENTIAL AND PROPRIETARY INFORMATION WHICH IS THE
             PROPERTY OF MENTOR GRAPHICS CORPORATION OR ITS LICENSORS
//
//
// Running on Linux j_abba@grace.encs.concordia.ca #1 SMP Tue Sep 12 10:10:26 CDT 2017 3.10.0-693.2.2.e17.x86_64 x86_64
// Start time Fri Oct 6 17:44:11 2017
# Info: [9566]: Logging session transcript to file /nfs/home/j/j abba/Modelsim/LAB1/FPGA ADV/precision.log
# COMMAND: new_project -name 32bitalu -folder /nfs/home/j/j_abba/Modelsim/LAB1/FFGA_ADV -createimpl_name 32bitalu_impl_1
# Info: [9574]: Input directory: /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV
# Info: [9569]: Moving session transcript to file /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/precision.log
# Info: [9555]: Created project /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu.psp in folder /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV.
# Info: [9531]: Created directory: /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_impl_1.
# Info: [9554]: Created implementation 32bitalu_impl_1 in project /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu.psp.
# Info: [9575]: The Results Directory has been set to: /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_impl_1/
# Info: [9566]: Logging project transcript to file /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_impl_1/precision.log
# Info: [9566]: Logging suppressed messages transcript to file /nfs/home/j/j_abba/Modelsim/LAB1/FFGA_ADV/32bitalu_impl_1/precision.log.suppressed
# Info: [9550]: Activated implementation 32bitalu_impl_1 in project /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_nsp.
new_project -name 32bitalu -folder /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV -createimpl_name 32bitalu_impl_1
# COMMAND: add_input_file {../Code/alu32bit.vhd}
add_input_file {../Code/alu32bit.vhd}
# COMMAND: add_input_file {../Code/alu1bitmostsignificant.vhd ../Code/alu1bit.vhd}
add input file {../Code/alulbitmostsignificant.vhd ../Code/alulbit.vhd}
# COMMAND: setup_design -manufacturer Xilinx -family "VIRTEX-II Pro" -part 2VP30ff896 -speed -7
# Info: [15298]: Setting up the design to use synthesis library "xcv2p.syn"
# Info: [575]: The global max famout is currently set to 10000 for Xilinx - VIRTEX-II Pro.
# Info: [15324]: Setting Part to: "2VP30ff896".
# Info: [15325]: Setting Process to: "7"
# Info: [7512]: The place and route tool for current technology is ISE.
setup_design -manufacturer Xilinx -family "VIRTEX-II Pro" -part 2VP30ff896 -speed -7
# COMMAND: setup_design -frequency 100 -max_fanout=10000
# Info: [575]: The global max famout is currently set to 10000 for Xilinx - VIRTEX-II Pro.
setup_design -frequency 100 -max_fanout=10000
# COMMAND: compile
# Info: [3022]: Reading file: /CMC/tools/mentor/precision/Mgc_home/pkgs/psr/techlibs/xcv2p.syn.
# Info: [634]: Loading library initialisation file /CMC/tools/mentor/precision/Mgc_home/pkgs/psr/userware/xilinx_rename.tcl
# Info: XILINX
# Info: [40000]: vhdlorder, Release 2016a.7
# Info: [40000]: Files sorted successfully.
# Info: [40000]: hdl-analyse, Release RTLC-Precision 2016a.7
# Info: [42502]: Analysing input file "/nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/../Code/alu1bit.vhd" ...
# Info: [42502]: Analysing input file "/nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/../Code/alu1bitmostsignificant.vhd" ...
# Info: [42502]: Analysing input file "/nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/../Code/alu32bit.vhd" ...
# Warning: [43642]: "/nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/../Code/alu32bit.vhd", line 183:
# Design unit LAB1 is already present in library work. Overwriting old definition of this design unit
# Info: [659]: Top module of the design is set to: lab1.
# Info: [657]: Current working directory: /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_impl_1.
# Info: [40000]: RTLC-Driver, Release RTLC-Precision 2016a.7
# Info: [40000]: Last compiled on Jun 2 2016 06:11:46
# Info: [44512]: Initializing...
# Info: [44504]: Partitioning design ....
# Info: [40000]: RTLCompiler, Release RTLC-Precision 2016a.7
# Info: [40000]: Last compiled on Jun 2 2016 06:47:43
# Info: [44512]: Initializing...
# Info: [44522]: Root Module work.alu32bit(lab1) (configuration lab1): Pre-processing...
# Info: [44506]: Module work.alu1bit(lab1): Pre-processing..
# Info: [44506]: Module work.alulbitmostsignificant(lab1): Pre-processing...
# Info: [44508]: Module work.alulbit(lab1): Compiling...
# Info: [44508]: Module work.alu1bitmostsignificant(lab1): Compiling..
# Info: [44523]: Root Module work.alu32bit(lab1){configuration lab1}: Compiling...
# Info: [44842]: Compilation successfully completed.
# Info: [44856]: Total lines of RTL compiled: 2558.
# Info: [44835]: Total CPU time for compilation: 0.0 secs.
# Info: [44513]: Overall running time for compilation: 1.0 secs.
# Info: [657]: Current working directory: /nfs/home/j/j_abba/Modelsim/LAB1/FPGA_ADV/32bitalu_impl_1.
# Info: [15330]: Doing rtl optimisations.
# Info: [660]: Finished compiling design.
compile
```

I got one warning during compilation which I believe is minor since it was my second time compiling the warning was about overwriting an older version of the 'LAB1' (name of my architecture) design unit.

# **Conclusion**

In conclusion, in this lab I successfully implemented a single-cycle 32-bit ALU using structural VHDL following a well-established design of cascading 1-bit ALUs and adding the overflow/set functionality to the MSB 1-bit ALU.

The code was then compiled and simulated using Modelsim which allowed confirming its functionality and correctness. Having done that an RTL schematic was generated to obtain a physical representation of the entity and using the precision log we were able to identify possible mistakes and errors.

After mapping the inputs and outputs to test the design on the FPGA, I noticed some weird behavior with the unmapped bits. I would have expected them to default to 'pull down' or 'pull up' but they seemed to have unexpected behavior (perhaps this was just my board).

Finally, my design approach led me to a solid understanding of ALUs and to appreciate the expressiveness of VHDL (i.e. if I hadn't used structural). In the report I presented some arguments as to the advantages of my approach but certainly there are advantages to take the "easier" route.

Regardless, in the future it will be easy to instantiate my 32-bit ALU and use it as part of a larger design of a CPU.